

٠.,

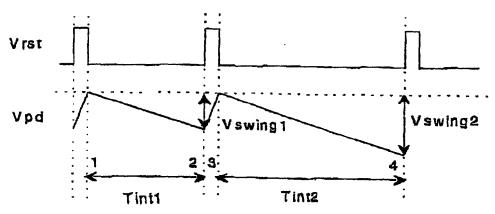


Figure 2 Voltage Swing on Photodiode


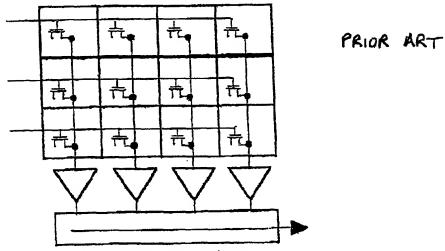


Figure 3 Multiplex Readout

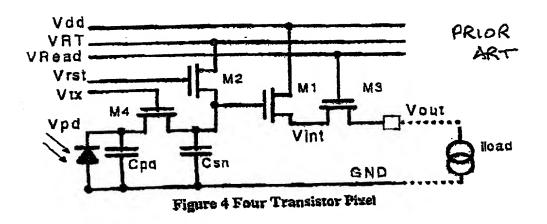




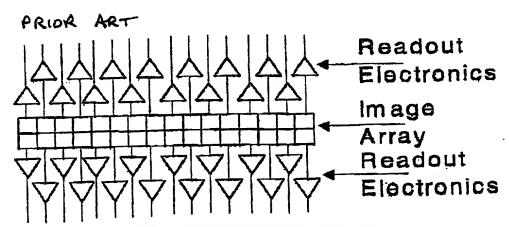


Figure 5 Sophisticated Linear Array

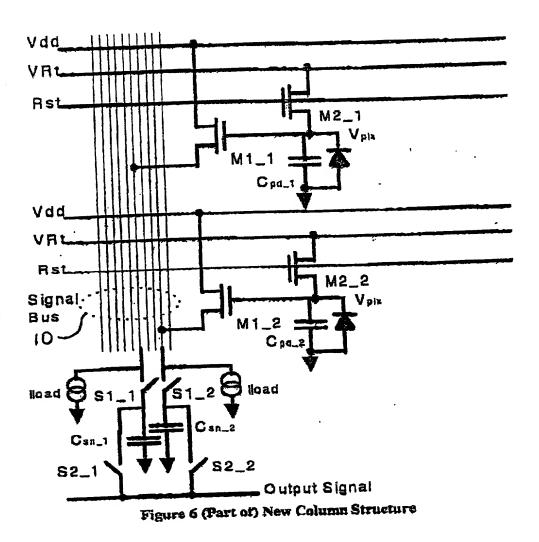

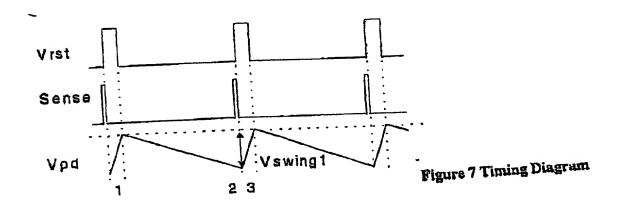

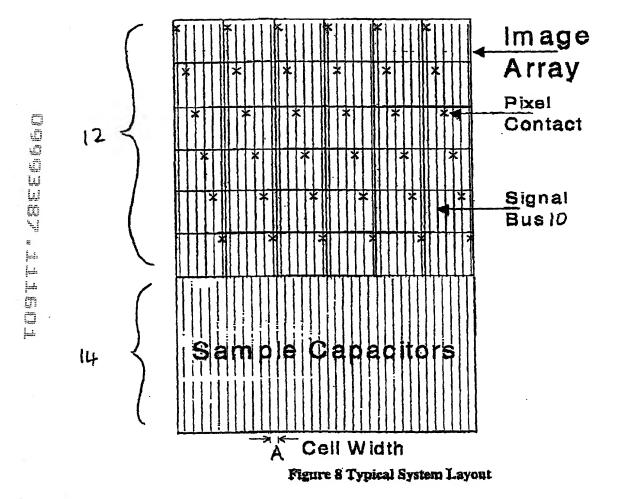

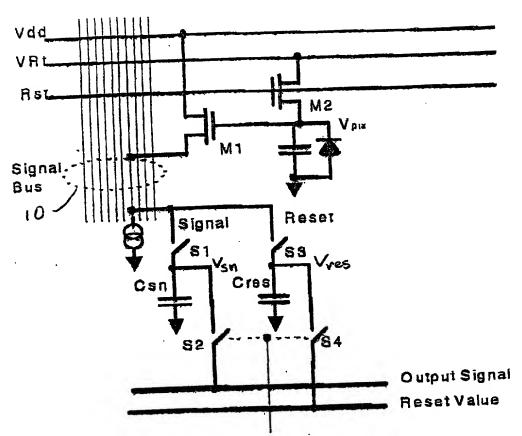


Figure 9 Improved Circuit - Offset Cancellation

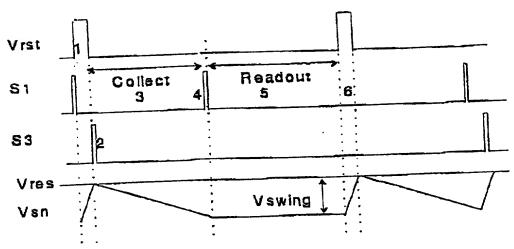


Figure 10 Offset Cancellation - Timing diagram

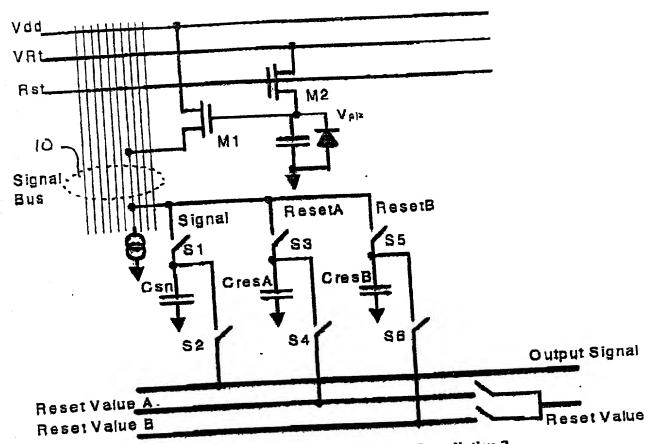


Figure 11 Improved Circuit - Offset Cancellation 2


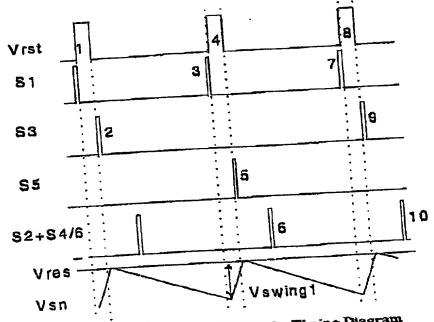


Figure 12 Offset Compensation 2 - Timing Diagram

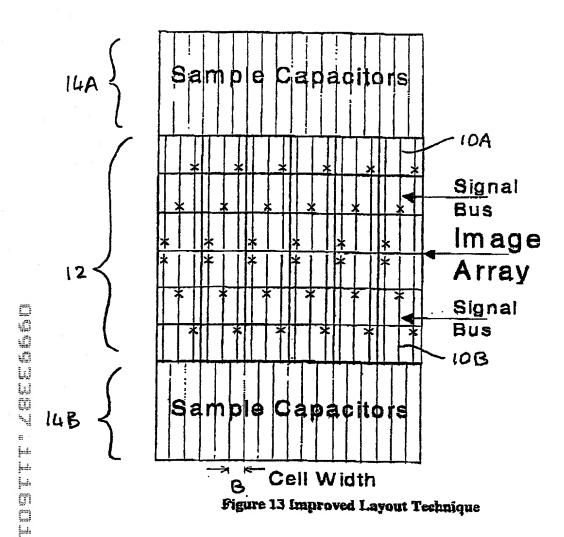

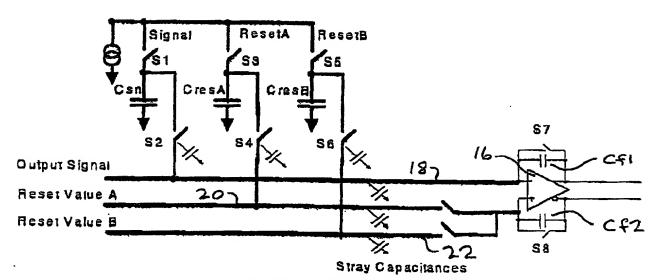


Figure 14 Preferred Readout Amplification